

Printed Pages: 2	
Name: <u>Ankit Kumar</u> Student University Roll No.: <u>1210 432082</u> School of Engineering First Sessional Examination, Even Semester (AS: 2021-22) B. Tech: CSE Year: 1 Semester: II	
Course Title: Basic Electrical Engineering Course Code: BEE3201	Max Marks: 30 Time: 1 hr

Instructions if any: Read the question Carefully.

SECTION 'A'		Course Objective	Marks
Q.N.1. Attempt all parts of the following:			
a)	Define 'linear' & 'nonlinear' circuit elements.	CO1	1
b)	What is an ideal current source?	CO1	1
c)	State Millman's Theorem.	CO1	1
d)	What is Quality Factor?	CO2	1
e)	Define Peak Factor and Form Factor.	CO2	1
SECTION 'B'		Course Objective	Marks
Q.N.2. Attempt any two parts of the following:			
a)	Explain Star to Delta transformation to solve network problems.	CO1	7.5
b)	State and explain Maximum Power transfer theorem to solve network problems, and also write two applications.	CO1	7.5
c)	Prove that the maximum value of current is equal to root two times of rms value.	CO2	7.5
d)	Define: Real, Reactive & Apparent power in AC circuit.	CO2	7.5


IP.T.O.

SECTION 'C'

Course Objecti ve	Mar ks
-------------------------	-----------


Q.N.3. Attempt any one part of the following:

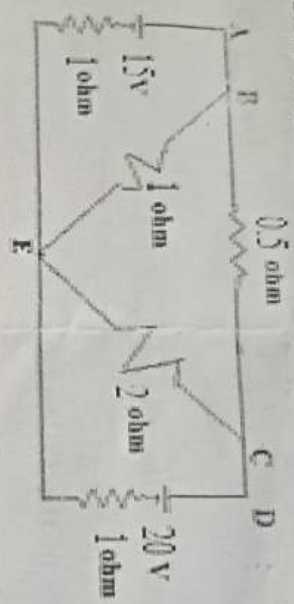By using nodal analysis, find the current in all resistive branches.



CO1 10

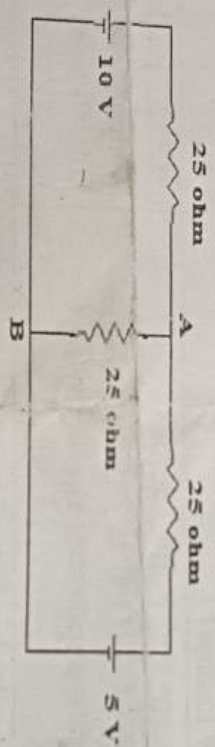Calculate the current in branch AB in given circuit, using Thevenin theorem.



CO1 10

Prove that the average power consumed in pure inductive circuit is zero.

CO2 10

Table 1: Mapping between COs and questions  
(Number of COs may vary from course to course)

COs	Questions Numbers	Total Marks
CO1	1 (a, b, c) 2(a, b) 3(a, b)	38
CO2	1(d, e) 2(c, d) 3(c)	27

Name: Student

First B. Tech Course Title