

S.No. : 47

BCS 2303

No. of Printed Pages : 05

Following Paper ID and Roll No. to be filled in your Answer Book.

PAPER ID : 23205

Roll  
No.

--	--	--	--	--	--	--	--	--	--

## B. Tech. Examination 2019-2020

(Odd Semester)

### DIGITAL LOGIC DESIGN

*Time : Three Hours] – [Maximum Marks : 60*

**Note :-** Attempt all questions.

#### SECTION – A

1. Attempt all parts of the following :  $1 \times 8 = 8$

(a) Subtract following unsigned number using 2's complement :

(i)  $11011 - 11001$

(ii)  $101010 - 101011$

(b) Define weighted and unweighted codes with example.

(c) Why 2's complement representation is used in real life?

**[P. T. O.]**

- (d) Draw a digital circuit of 2, two bit binary multiplier.
- (e) Differentiate between latch and flip-flop.
- (f) Explain races in asynchronous sequential circuit.
- (g) Differentiate between moore and Mealy machines.
- (h) Define fundamental mode operation.

### SECTION – B

2. Attempt any two parts of the following :  $6 \times 2 = 12$

- (a) Represent following number in IEEE single and double precision format :
  - (i)  $(105.625)_{10}$
  - (ii)  $(-23.25)_{10}$
- (b) What is lookahead carry adder? Discuss its advantage and disadvantage. Design lookahead carry adder and draw the circuit for it.
- (c) A sequential circuit with 2 Dff A and B two inputs x and y and output z is specified by the following next state and output equation :

$$A(t+1) = X'Y + XA$$

$$B(t+1) = X'B + XA$$

$$Z = B$$

Draw the logic diagram, list state table and state diagram of the circuit.

- (d) Differentiate between PAL and PLA implement following boolean function using PLA.

$$F_1 = AB' + AC + A'BC'$$

$$F_2 = (AC + BC)'$$

### SECTION - C

**Note:-** Attempt all questions. Attempt two parts from each questions.  $8 \times 5 = 40$

3. (a) The Hamming code 101101101 is received with even parity correct errors if any.
- (b) What is Universal gates? Realize OR gate using NAND gate only.
- (c) Minimize following four variable boolean function using K map.

**[P. T. O.]**

$$F(A, B, C, D) = \sum m(4, 5, 6, 7, 8, 12) + \sum d(0, 1, 2, 3, 9, 11, 14)$$

4. (a) Design Decimal Odder.
- (b) What is encoder? Design Octal to Binary encoder. Also explain priority encoder in detail.
- (c) Design 4 x 1 multiplexer. Implement following boolean expression using 8 x 1 MUX.

$$F(A, B, C, D) = \sum m(0, 1, 3, 4, 8, 9, 15)$$

5. (a) What is race around condition in J-K flip-Flop? How to resolve it?
- (b) What do you understand by registers. Explain classification of register in detail with logic circuit.
- (c) Design 4-bit ripple counter using suitable waveform.
6. (a) What do you understand by Hazards? Explain in detail.
- (b) An asynchronous sequential circuit is described by the excitation and output functions.

$$Y = X_1 X_2^1 + (x_1 + x_2^1) y$$

$$z = y$$

- (i) Draw the logic diagram of the circuit.
  - (ii) Derive the transition table and output map.
  - (iii) Obtain flow table.
- (c) What is VHDL? Write VHDL code for traffic light controller.

\*\*\*