

No. of Printed Pages : 05

Following Paper ID and Roll No. to be filled in your Answer Book.

PAPER ID : 33402Roll
No.

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

B. Tech. Examination 2022-23**(Even Semester)****BASIC ELECTRONICS ENGINEERING****Time : Three Hours]****[Maximum Marks : 60****Note :-** Attempt all questions.**SECTION-A**

1. Attempt all parts of the following : $8 \times 1 = 8$
- (a) Which type of impurity is added to make n-type semiconductor?
 - (b) Draw the VI characteristics of an ideal diode.
 - (c) Write down the biasing condition of a BJT for active mode.
 - (d) What is the function of SiO_2 layer in MOSFET?
 - (e) Draw the circuit diagram of voltage follower.

[P. T. O.]

- (f) For an OP-amp if $A_d = 5 \times 10^5$ and $AC = 50$. Find CMRR.
- (g) Write down the truth table for two input NOR gate.
- (h) What is the value of $X + X'$?

SECTION - B

2. Attempt any two parts of the following : $2 \times 6 = 12$

- (a) A bridge rectifier circuit with $R_L = 200 \text{ K}\Omega$ is is given an input of 230V, 50 Hz from power mains through a transformer having turn ratio 4 : 1. Calculate I_{dc} , I_{rms} , ripple, factor, P_{dc} , P_{ac} and rectification efficiency. Neglect the diode and secondary winding resistance.
- (b) Sketch and explain the input and output characteristics of transistor in CE configuration. Why CE configuration is most widely used for amplification?
- (c) Perform the following conversion :
- (i) $(10.265)_{10} = (?)_2$
- (ii) $(475.25)_8 = (?)_{10}$

(iii) $(B2C.D6)_{16} = (?)_2$


(iv) $(736.25)_8 = (?)_{16}$

- (d) Draw the circuit of a difference amplifier using OP-AMP. Also derive the expression for output voltage.


SECTION - C

Note :- Attempt all questions. Attempt any two parts from each question. $5 \times 8 = 40$

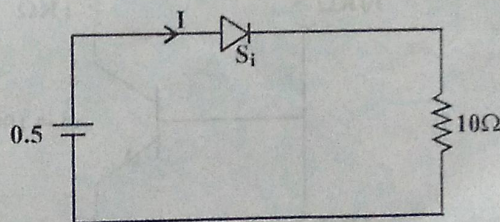3. (a) Explain worknig of PN junction diode in forward biased condition. Calculate the current I for the network given below :




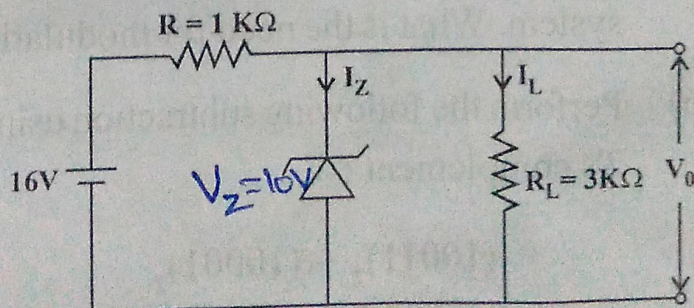- (b) Explain Zener breakdown mechanism in a reversed biased diode. For the network given below find V_0 and I_Z :



[P. T. O.]

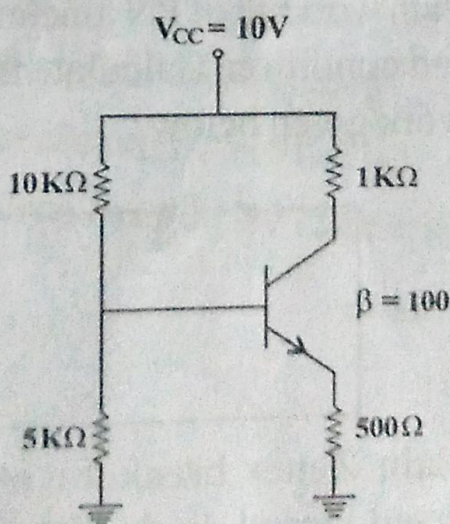- (c) Explain the working of LED with neat diagram. What are the advantages of LED?
4. (a) Explain the input and output characteristics of a BJT in CE configuration.
- (b) Explain the construction and drain characteristics of N-channel E-MOSFET.
- (c) For the following voltage divider circuit find the I and V_{CE} . Assume germanium transistor :




5. (a) Explain the block diagram of communication system. What is the need for modulation?
- (b) Perform the following subtraction using 1's and 2's complement :

$$(10011)_2 - (10001)_2$$

- (c) What are the universal gates? Reduce the following function using K-map and implement the reduced function with basic gate :

$$F(A B C D) = \Sigma (0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$$

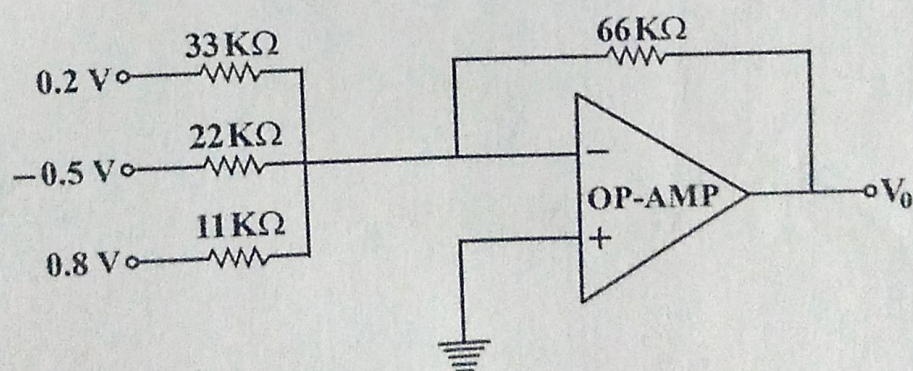6. (a) What do you understand by CMRR? Enlist the characteristics of ideal OP-AMP.
- (b) Derive the output expression for the inverting summing op-amp. Find the output voltage for the following network :



- (c) Which type of feedback is used for the oscillation? Explain the principle of oscillator and describe the Barkhausen criterion.