

Name: \_\_\_\_\_ Printed Pages: 1  
 Student University Roll No.: \_\_\_\_\_  
 School of Engineering  
 First Sessional Examination, Odd Semester (AS: 2023-24)  
 B. Tech: CSE  
 Year: 1<sup>st</sup> Semester: 1<sup>st</sup>  
 CSIA-1J  
 Course Title: Basic Electronics Engineering M.M.: 30  
 Course Code: NEC 4101 Time: 1 hr


Instructions if any: Read the question Carefully.

SECTION 'A'		Course Objective	Marks
Q.N.1. Attempt all parts of the following:			
a)	Draw the VI characteristics of Ideal Diode.	CO1	1
b)	What do you mean by donor impurity?	CO1	1
c)	What is PIV of the diode?	CO1	1
d)	Draw the energy band diagram of semiconductor?	CO1	1
e)	Write down the minority and majority carrier in N type semiconductors.	CO1	1

SECTION 'B'		Course Objective	Marks
Q.N.2. Attempt any two parts of the following:			

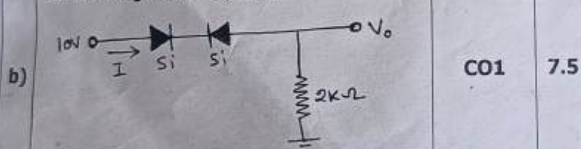a) Explain the working of p-n junction diode in reverse biased condition.

Find the output voltage  $V_o$  and current  $I$  in the following diode network.




c) What do you mean by rectifier? Explain the working of Bridge full wave rectifier in detail.

d) In a center tapped rectifier the voltage across half of the secondary winding is given as  $200 \sin \omega t$ . Find  $I_{dc}$ ,  $I_{rms}$  & ripple factor(r). Assume  $R_L = 20 \text{ k}\Omega$  and  $r_o = 20 \Omega$


SECTION 'C'  
 Q.N.3. Attempt any one part of the following

a) Explain construction and working of LED.

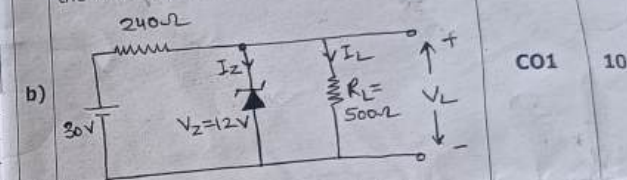b) Explain Zener breakdown mechanism. For the following circuit find  $I_L$ ,  $I_Z$ ,  $V_L$



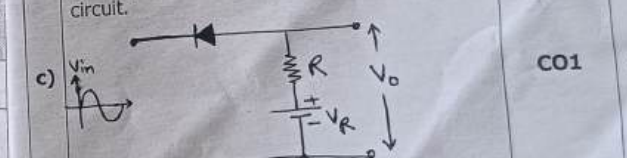c) What do you mean by clipper circuits? Find the output waveform of the following clipper circuit.



Total Marks

Table 1: Mapping betw 3(b,c,e)  
 (Number of COs)

COs	Question
CO1	1(a,b,c,d,e), 2(a,b,c)


Total Marks

53

12

Name: \_\_\_\_\_ Printed Pages: 1  
 Student University Roll No.: \_\_\_\_\_  
 School of Engineering  
 First Sessional Examination, Even Semester (AS: 2023-24)  
 B. Tech: CS-A1-1A to CS-A1-1F, CS-1K, CS-1L, IOTBC-1A, CCML-1A  
 Year: 1<sup>st</sup> Semester: 2<sup>nd</sup>  
 Course Title: Basic Electronics Engineering M.M.: 30  
 Course Code: NEC 4201 Time: 1 hr

Instructions: Read the question Carefully.

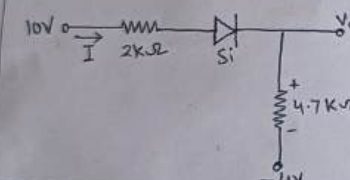SECTION 'A'		Course Objective	Marks
Q.N.1. Attempt all parts of the following:			
a)	What is donor impurity?	CO1	1
b)	Draw the energy band diagram of Insulator?	CO1	1
c)	Draw the VI characteristics of ideal diode.	CO1	1
d)	Write down the biasing condition for a transistor used in active mode.	CO2	1
e)	If $\beta = 98$ find the value of $\alpha$ .	CO2	1
SECTION 'B'		Course Objective	Marks
Q.N.2. Attempt any two parts of the following:			
a)	With neat diagram explain the working of p-n junction diode in Forward biased condition.	CO1	7.5
b)	Find the output voltage $V_o$ in the following diode network.	CO1	7.5
			
c)	What do you mean by rectifier? Explain the working of center tapped full wave rectifier.	CO1	7.5
d)	A Bridge rectifier circuit is supplied from 230 V, 50 Hz supply with a step down ratio of 3:1 to a resistive load of 10 KΩ. Diode forward resistance is 75 Ω while transformer secondary resistance is 10 Ω. Find	CO1	7.5

Find  $I_{rms}$  & ripple factor(r).

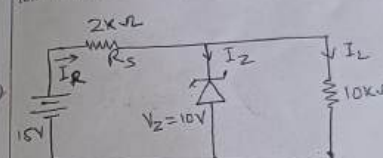
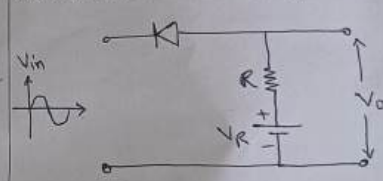
SECTION 'C'		Course Objective	Marks
Q.N.3. Attempt any one part of the following			
a)	Explain the working of PNP transistor?	CO2	10
b)	Explain Zener breakdown mechanism. For the following circuit find $I_L$ , $I_Z$ , $I_R$ & $V_L$ .	CO1	10
			
c)	What do you mean by clipper circuits? Find the output waveform of the following clipper circuit.	CO1	10
			

Table 1: Mapping between COs and questions  
 (Number of COs may vary from course to course)

COs	Questions Numbers	Total Marks
CO1	1(a,b,c,), 2(a,b,c,d), 3(b,c,)	53
CO2	1(d,e),3(a,)	12